

1. The circuit translates as follows:  $(A + B) \bar{B}$ .  
To be TRUE both factors must be TRUE. B must be equal to 0.  
Therefore, A must be equal to 1.

1. (1,0)

2. The circuit translates as follows:  $(\bar{X} Y) (Y \oplus \bar{Z})$ . It simplifies to:  
 $(X + \bar{Y})(YZ + \bar{Y}\bar{Z}) = XYZ + X\bar{Y}\bar{Z} + \bar{Y}YZ + \bar{Y}\bar{Y}\bar{Z} =$   
 $XYZ + X\bar{Y}\bar{Z} + \bar{Y}\bar{Z}(X + 1) = XYZ + \bar{Y}\bar{Z}$

2.  $XYZ + \bar{Y}\bar{Z}$ 

3. The expression simplifies as follows:

$$\begin{aligned} \bar{A}B + \bar{A}C + \bar{A}\bar{B} + \bar{B}C + A\bar{C} + \bar{B}\bar{C} &= \\ (\bar{A}B + \bar{A}\bar{B}) + (\bar{B}C + \bar{B}\bar{C}) + (A\bar{C} + \bar{A}\bar{C}) &= \\ \bar{A}(B + \bar{B}) + \bar{B}(C + \bar{C}) + \bar{C}(A + \bar{A}) &= \\ \bar{A} + \bar{B} + \bar{C} = \overline{ABC} \quad (\text{note that } \bar{A}\bar{B}\bar{C} \text{ is not equivalent}) & \end{aligned}$$

3.  $\overline{ABC}$ 

4. By definition a simple path is a path with no vertex repeated. Choice A is not a valid path. Choice B has vertex B repeated. Choice C is a simple path. Choice D is not a valid path.

4. C

5. A "1" is placed in the matrix when a path exists. Otherwise, the matrix contains a "0".

	A	B	C	D
A	1	1	0	1
B	1	0	1	1
C	0	0	0	1
D	0	0	1	0

5. The matrix as shown at the left.