
Intermediate Division

Short Problems

1. Digital Electronics

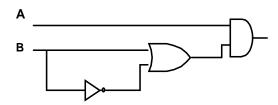

List all of the following statements that are true about the circuit above.

- a. It is TRUE for all possible inputs.
- b. It is FALSE for all possible inputs
- c. It is TRUE only when the two inputs are different.
- d. It is sometimes TRUE when the two inputs are different.
- e. It is FALSE whenever B is TRUE.

2. Prefix/Postfix

Convert the following postfix expression into prefix.

$$AAB + CAB / - / *$$

3. Prefix/Postfix

The volume of a sphere is given by the formula $V=4/3 \pi R^3$. Translate the formula, as written above, into prefix.

4. Data Structures

Consider the following operations on an initially empty queue. If a POP is now performed, what value would be popped?

PUSH	(B)	≯ PUSH	(D)
PUSH	(I)	POP	(X)
PUSH	(N)	PUSH	(S)
POP	(X)	POP	(X)

5. Data Structures

Insert the key "VULCAN" into the following binary search tree.

What is the new external path length?

